

## EE23BTECH11047 - Deepakreddy P

**44** The switch  $S_1$  was closed and  $S_2$  was open for a long time. At  $t=0$ , switch  $S_1$  is opened and  $S_2$  is closed, simultaneously. The value of  $i_c(0^+)$ , in amperes, is (GATE EC 44)

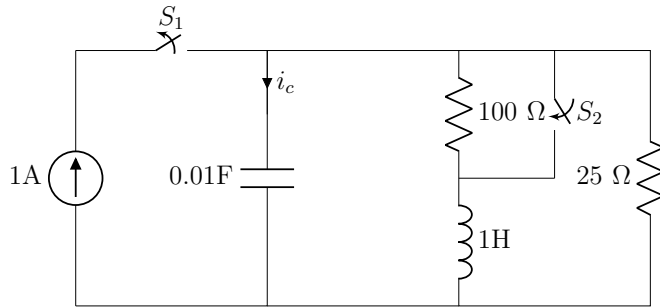
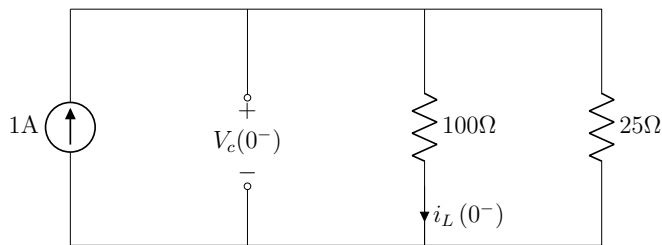


Fig. 1. Circuit 1

**Solution:**

1) Switch  $S_1$  was closed and  $S_2$  was open

Fig. 2.  $S_1$  is closed and  $S_2$  is open

$$R_{eff} = \frac{25(100)}{(25 + 100)} \Omega \quad (1)$$


$$R_{eff} = 20 \Omega \quad (2)$$

$$V_c(0^-) = 1(R_{eff}) \quad (3)$$

$$V_c(0^-) = 20V \quad (4)$$

2) Switch  $S_1$  is open and  $S_2$  was closed

At  $t = 0^+$  The capacitor is charged. Thus, it acts as a voltage source. The inductor acts as the current source.

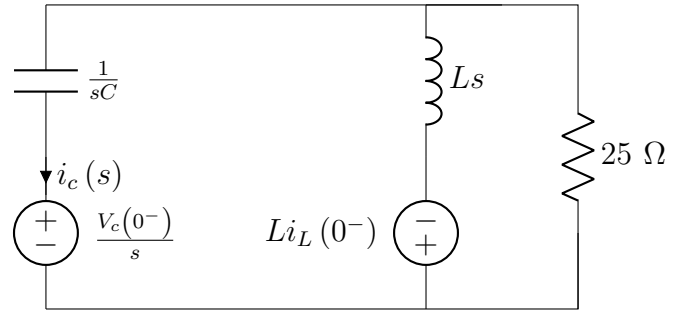Fig. 3.  $S_1$  is open and  $S_2$  is closed

By Superposition Theorem  
Case (i):

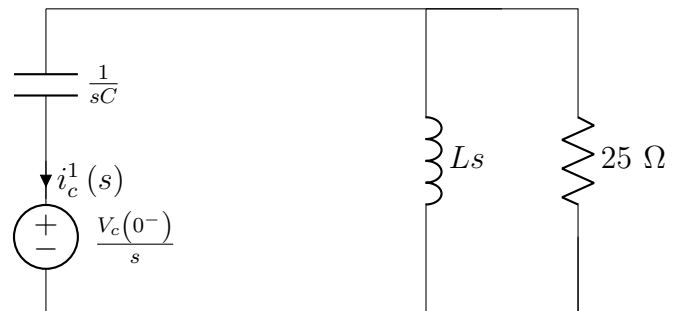


Fig. 4. Circuit 4

$$\left( \frac{25(Ls)}{25 + Ls} + \frac{1}{sC} \right) i_c^1(s) + \frac{V_c(0^-)}{s} = 0 \quad (5)$$

$$i_c^1(s) = -\frac{V_c(0^-)}{s} \left( \frac{25sC + LCs^2}{25LCs^2 + Ls + 25} \right) \quad (6)$$

$$i_c^1(s) = -\left( \frac{5 + 0.2s}{0.25s^2 + s + 25} \right) \quad (7)$$

Case (ii):

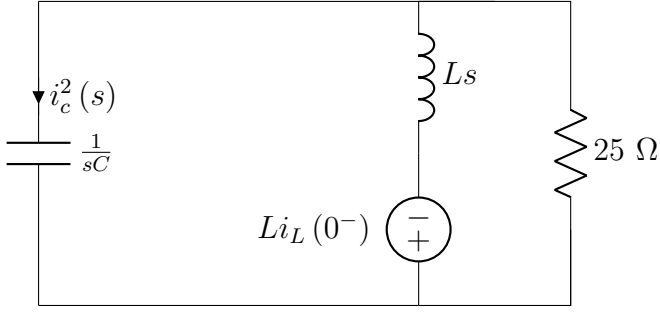


Fig. 5. Circuit 4

$$Li_L(0^-) + \left( \frac{25}{25sC + 1} + Ls \right) i_c^2(s) = 0 \quad (8)$$

$$0.2 = - \left( \frac{25LCs^2 + Ls + 25}{25sC + 1} \right) i_c^2(s) \quad (9)$$

$$i_c^2(s) = - \left( \frac{0.05s + 0.2}{0.25s^2 + s + 25} \right) \quad (10)$$

From eq (7) and eq (10)

$$i_c(s) = i_c^1(s) + i_c^2(s) \quad (11)$$

$$i_c(s) = - \left( \frac{0.25s + 5.2}{0.25s^2 + s + 25} \right) \quad (12)$$

Using Inverse Laplace Transform

From eq (12)

$$i_c(t) = -e^{-2t} \left( \cos(4\sqrt{6}t) + \frac{18.8}{4\sqrt{6}} \sin(4\sqrt{6}t) \right) \quad (13)$$

$$i_c(0^+) = -1A \quad (14)$$

Parameter	Description	Remarks
$V_c(0^-)$	Voltage across capacitor when $t < 0$	20V
$i_L(0^-)$	current across inductor when $t < 0$	0.2
$i_L(0^+)$	current across inductor when $t > 0$	0.2
$C$	Capacitance	0.01F
$L$	Inductance	1H

TABLE I  
PARAMETERS

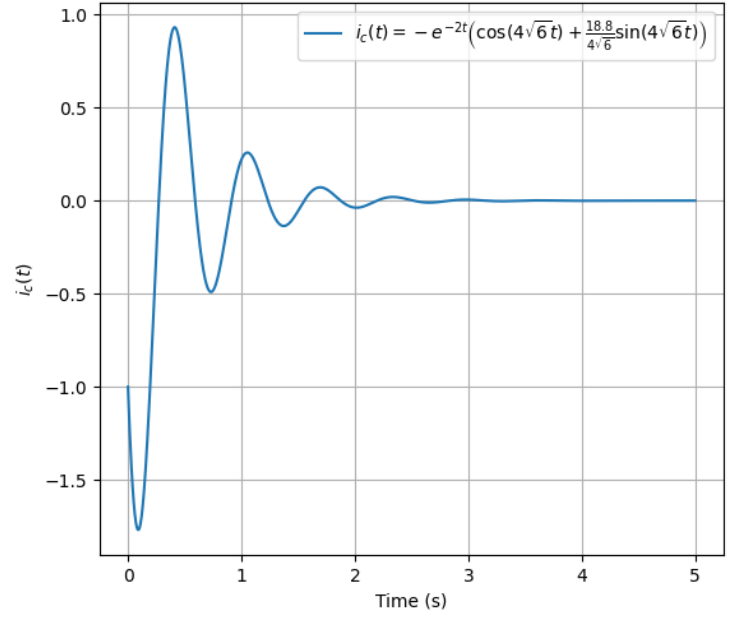


Fig. 6. Plot of  $i_c(t)$  vs time

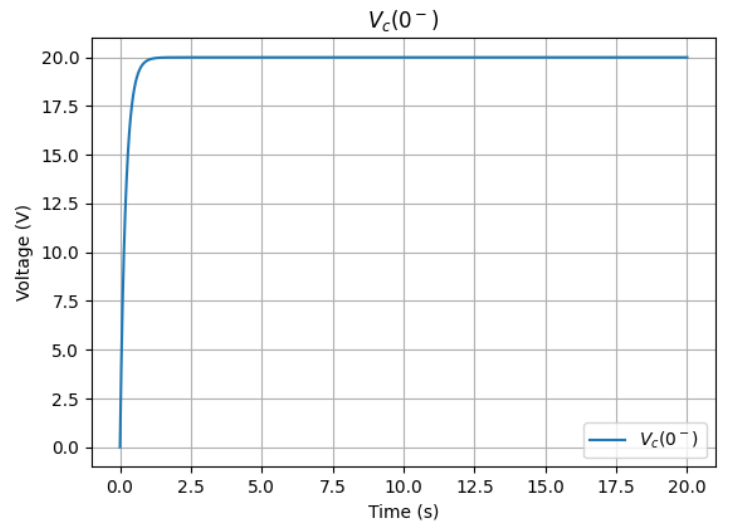


Fig. 7. Plot of  $V_c(0^-)$  vs time